

Basics of Logic Design: Boolean Algebra, Logic Gates

Computer Science 104

Administrative

- **Homework #3 Due tonight**
- **Midterm I Monday in class, open book, open notes**
 - **Book/notes for instruction reference mainly, don't rely them for other things**

Today's Lecture


Outline

- Building the building blocks...
- Logic Design
 - Truth tables, Boolean functions, Gates and Circuits

Reading

- 4.2 of text, but we are going into more detail than the text
- any other online resource you can find

What We've Done, Where We're Going

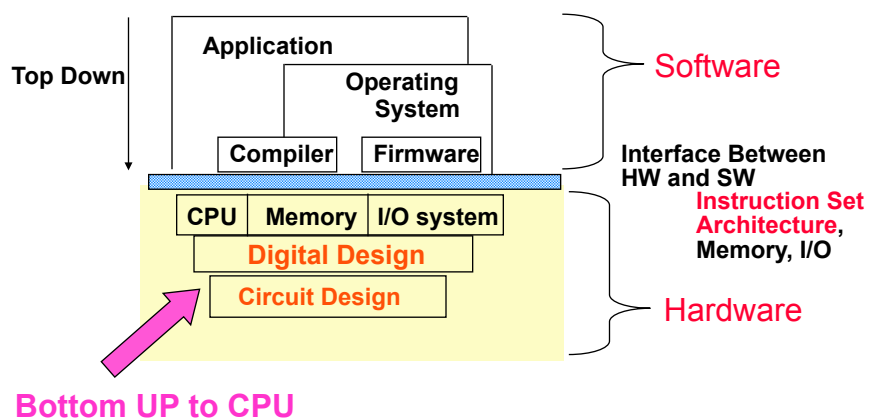

Digital Design

- Logic Design, Switching Circuits, Digital Logic

Recall: Everything is built from transistors

- A transistor is a switch
- It is either on or off
- **On** or **off** can represent **True** or **False**

Given a bunch of bits (0 or 1)...

- Is this instruction a movl or a je?
- What register do I read?
- How do I add two numbers?
- **Need a method to reason about complex expressions**

Boolean Algebra

- Boolean functions have arguments that take two values ($\{T,F\}$ or $\{1,0\}$) and they return a single or a set of ($\{T,F\}$ or $\{1,0\}$) value(s).
- Boolean functions can always be represented by a table called a “**Truth Table**”
- Example: $F: \{0,1\}^3 \rightarrow \{0,1\}^2$

a	b	c	f_1, f_2
0	0	0	0 1
0	0	1	1 1
0	1	0	1 0
0	1	1	0 0
1	0	0	1 0
1	1	0	0 1
1	1	1	1 1

Boolean Functions

- **Example Boolean Functions: NOT, AND, OR, XOR, ...**

a	NOT (a)
0	1
1	0

a	b	AND (a,b)
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR (a,b)
0	0	0
0	1	1
1	0	1
1	1	1

a	b	XOR (a,b)
0	0	0
0	1	1
1	0	1
1	1	0

a	b	XNOR (a,b)
0	0	1
0	1	0
1	0	0
1	1	1

a	b	NOR (a,b)
0	0	1
0	1	0
1	0	0
1	1	0

Boolean Functions and Expressions

- **Boolean algebra notation:** Use * for AND, + for OR, ~ for NOT.

➤ NOT is also written as A' and \bar{A}

- Using the above notation we can write Boolean expressions for functions

$$F(A, B, C) = (A * B) + (\sim A * C)$$

- We can evaluate the Boolean expression with all possible argument values to construct a truth table.
- What is truth table for F?

Boolean Function Simplification

- Boolean expressions can be simplified by using the following rules (bitwise logical):

- $A * A = A$
- $A * 0 = 0$
- $A * 1 = A$
- $A * \sim A = 0$

- $A + A = A$
- $A + 0 = A$
- $A + 1 = 1$
- $A + \sim A = 1$

- $A * B = B * A$
- $A * (B + C) = (B + C) * A = A * B + A * C$

Boolean Function Simplification

a	b	c	f_1, f_2
0	0	0	0 1
0	0	1	1 1
0	1	0	0 0
0	1	1	1 0
1	0	0	0 0
1	0	1	1 0
1	1	0	0 1
1	1	1	1 1

$$f_1 = \sim a * \sim b * c + \sim a * b * c + a * \sim b * c + a * b * c$$

$$f_2 = \sim a * \sim b * \sim c + \sim a * \sim b * c + a * b * \sim c + a * b * c$$

Simplify these functions...

Boolean Functions and Expressions

- **The Fundamental Theorem of Boolean Algebra:** Every Boolean function can be written in disjunctive normal form as an OR of ANDs (**Sum-of products**) of it's arguments or their complements.

“Proof:” Write the truth table, construct sum-of-product from the table.

a	b	XNOR(a,b)
0	0	1
0	1	0
1	0	0
1	1	1

$$\text{XNOR} = (\sim a * \sim b) + (a * b)$$

Boolean Functions and Expressions

- **Example-2:**

a	b	c	f ₁ , f ₂
0	0	0	0 1
0	0	1	1 1
0	1	0	1 0
0	1	1	0 0
1	0	0	1 0
1	1	0	0 1
1	1	1	1 1

$$f_1 = \sim a * \sim b * c + \sim a * b * \sim c + a * \sim b * \sim c + a * b * c$$

$$f_2 = \sim a * \sim b * \sim c + \sim a * \sim b * c + a * b * \sim c + a * b * c$$







Applying the Theory

- Lots of good theory
- Can reason about complex boolean expressions
- Now we have to make it real...

Boolean Gates

- **Gates** are electronic devices that implement simple Boolean functions

Examples

      

Reality Check

- Basic 1 or 2 Input Boolean Gate 1- 4 Transistors

Pentium III

- Processor Core 9.5 Million Transistors
- **Total: 28 Million Transistors**

Pentium 4

- **Total: 42 Million Transistors**

Core2 Duo (two cores)

- **Total: 290 Million Transistors**


Corei7 (4 cores)

- **Total: 731 Million Transistors**

- Insert Tangent about what a transistor is...


Boolean Functions, Gates and Circuits

 - **Circuits** are made from a network of gates. (function compositions).



$$F = \sim a * b + \sim b * a$$

a	b	XOR(a,b)
0	0	0
0	1	1
1	0	1
1	1	0

 

Digital Design Examples

Input: 2 bits representing an unsigned number (n)

Output: n^2 as 4-bit unsigned binary number

Input: 2 bits representing an unsigned number (n)

Output: $3-n$ as unsigned binary number

Design Example

- Consider machine with 4 registers
- Given 2-bit input (register specifier, I_1, I_0)
- Want one of 4 output bits (O_3-O_0) to be 1
 - E.g., allows a single register to be accessed
- What is the circuit for this?


More Design Examples

- **X is a 3-bit quantity**
1. Write a logic function that is true if and only if X contains at least two 1s.
 2. Implement the logic function from problem 1. using only AND, OR and NOT gates. (Note there are no constraints on the number of gate inputs.) By implement, I mean draw the circuit diagram.
 3. Write a logic function that is true if and only if X, when interpreted as an unsigned binary number, is greater than the number 4.
 4. Implement the logic function from problem 3. using only AND, OR and NOT gates. (Note there are no constraints on the number of gate inputs.)

Parity Example

- The parity code of a binary word counts the number of ones in a word. If there are an even number of ones the parity code is 0, if there are an odd number of ones the parity code is 1. For example, the parity of 0101 is 0, and the parity of 1101 is 1.
- Construct the truth table for a function that computes the parity of a **four-bit word**. Implement this function using AND, OR and NOT gates. (Note there are no constraints on the number of gate inputs.)


Circuit Example: Decoder

 


I_1	I_0	Q_0	Q_1	Q_2	Q_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Circuit Example: 2x1 MUX

 
Multiplexor (MUX) selects from one of many inputs


 
$$\text{MUX}(A, B, S) = (A * S) + (B * \sim S)$$



Example 4x1 MUX

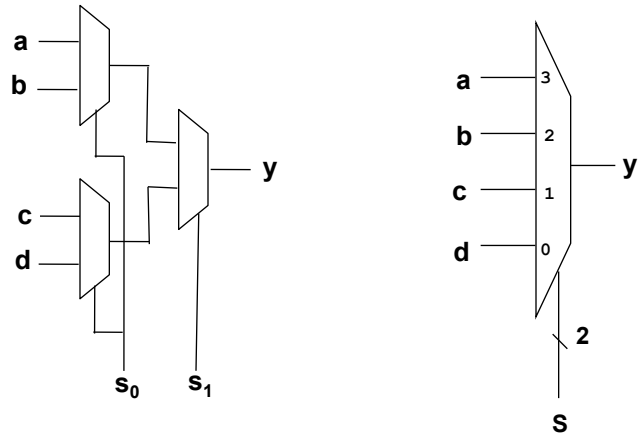

Arithmetic and Logical Operations in ISA

- What operations are there?
- How do we implement them?
 - Consider a 1-bit Adder

Summary

- Boolean Algebra & functions
- Logic gates (AND, OR, NOT, etc)
- Multiplexors

Reading

- 4.2 of text

DeMorgan's Laws

- $\sim(A+B) = \sim A * \sim B$
- $\sim(A*B) = \sim A + \sim B$

Example:

- $\sim C * \sim A * B + \sim C * A * \sim B + C * A * B + C * \sim A * \sim B$
- Use only XOR to represent this function