

Register File, Finite State Machines & Hardware Control Language

Avin R. Lebeck

Some slides based on those developed by Gershon Kedem, and by Randy Bryant and Dave O'Hallaron

Compsci 104 1

Administrivia

- Homework #4 is up, due Oct 20
- Midterm: Median 90
- May be late for office hours Thursday Morning
- May move Monday afternoon office hours

Read

- Sections 4.1-4.3 of text
- Pragmatic Logic (PDF on blackboard or through Library)


Today

- Review Logic Design
 - * Logisim demo (work through beginners guide)
- Memory: Latches, FlipFlops, Register file
- Finite State Machines: Sequential Circuits
- Hardware Control Language (if time)


Compsci 104 2

Review: Boolean Functions, Gates and Circuits

- **Circuits** are made from a network of gates. (function compositions).
- **Logisim demo**

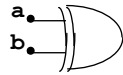

 $\text{XOR}(a, b) \quad F = \sim a * b + \sim b * a$

a	b	XOR(a, b)
0	0	0
0	1	1
1	0	1
1	1	0

 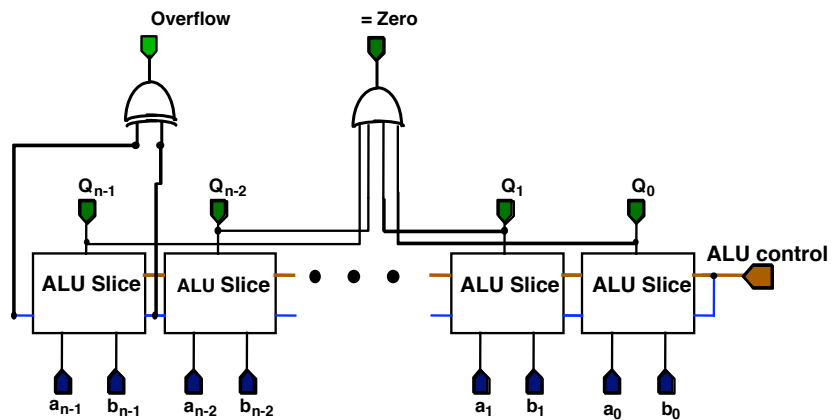

Compsci 104 3

Review: The ALU




Compsci 104 4

Review: Abstraction: The ALU



- General structure
- Two operand inputs
- Control inputs

 - We can build circuits for
 - * Multiplication
 - * Division
 - * They are more complex




Compsci 104 5

Review: Set-Reset Latch (Continued)

  


Compsci 104 6

Data Latch (D Latch)

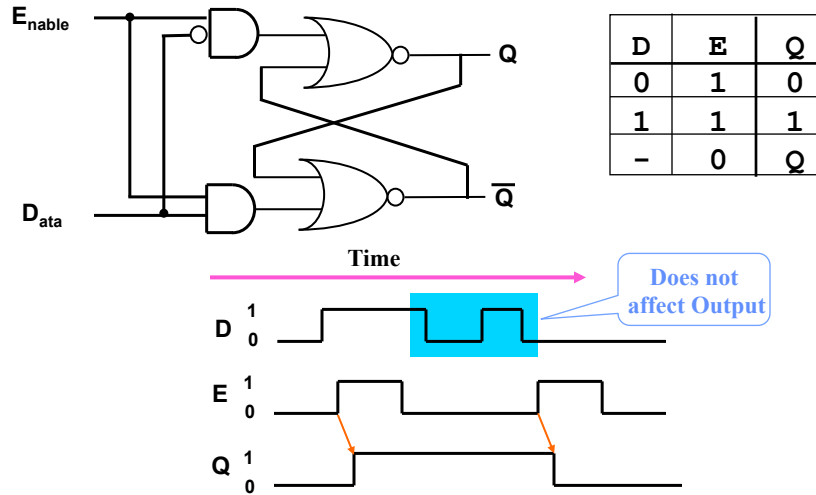

Compsci 104 7

D Flip-Flop

 

- On $C \uparrow$ D is transferred to the first D latch and the second is stable.
- On $C \downarrow$ the output of the first stage is transferred to the second (output), and the first stage is stable.
- Key: **Output changes only on the edge of a clock**
- Logisim demos

Compsci 104 8

Register File

- Register File = the set of locations for register values
 - * E.g., 32 32-bit registers
- How do I build a Register File using D Flip-Flops?
- What other components do I need?

Compsci 104 9


Register File

- Circuit to determine which of 32 registers?
- Circuit to get just the data from one of 32 registers?

Compsci 104 10


Tri-State Driver

 - The Tri-State driver is like a (one directional) switch:
 - * When the Enable is on (E=1) it transfers the input to the output.
 - * When the Enable is off (E=0) it disconnects the output.



D	E	Q
0	1	0
1	1	1
-	0	Z


Z :- High Impedance

 

Compsci 104 11


Bus Connections

 - The Bus: Many to many connections.
- Mutual exclusion: At most one Enable is on!
- Control must ensure this!
- Note: Bus sometimes used to denote multiple parallel wires



Compsci 104 12


Register Cells on a bus

 

One can “source” and “sink” from any cell on the bus by activating the right controls, **IE**--input enable, and **OE**--output enable.

Compsci 104 13


3-Port Register Cell

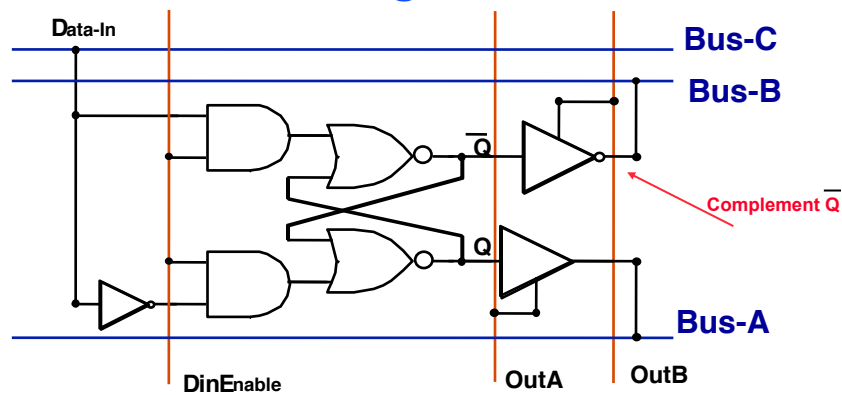


- Stores one bit of a register
- Can Read onto Bus-A & Bus-B and Write from Bus-C Simultaneously

Compsci 104 14


3-Port Register File

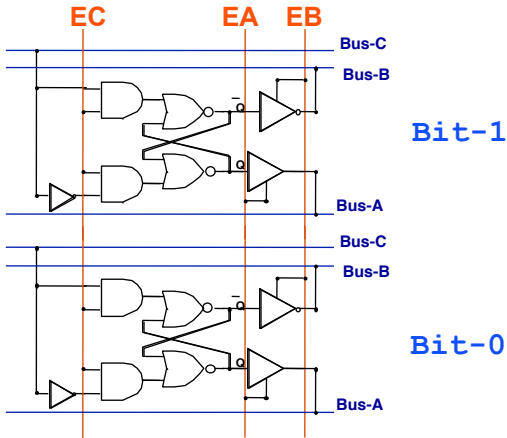

Address Decode Circuit

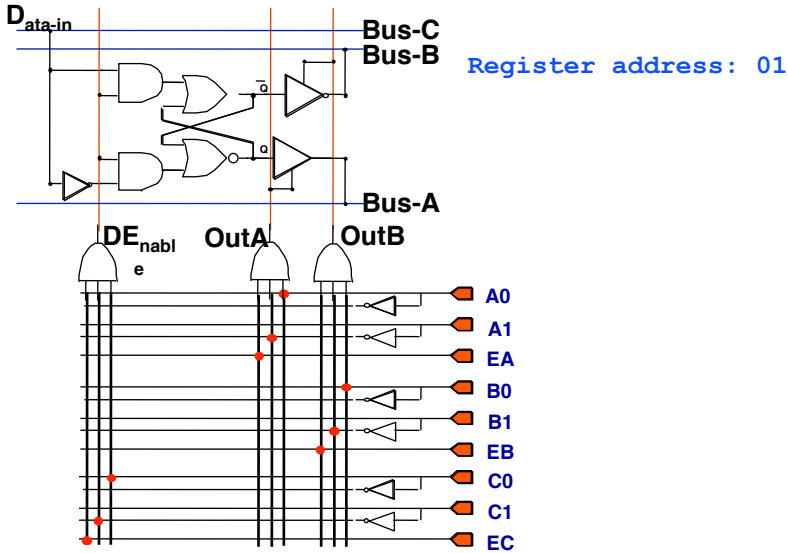

Register File (Four 4-bit Registers)

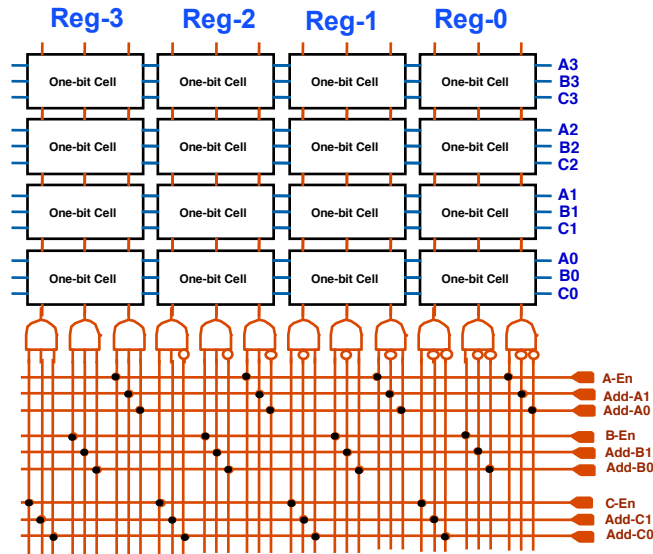

Compsci 104 17

Digital Logic Summary

- Given Boolean function, generate a circuit to “realize” the function.
- Constructed circuits that can **add** and **subtract**.
- The **ALU**: a circuit that can **add**, **subtract**, **detect overflow**, **compare**, and do **bit-wise operations (AND, OR, NOT)**
- **Shifter**
- **Memory Elements: SR-Latch, D Latch, D Flip-Flop**
- **Tri-state drivers & Bus Communication vs. MUX**
- **Register Files**
- **Control Signals** modify what circuit does with **inputs**
 - * ALU, Shift, Register Read/Write
- **Next**
 - * Finite State Machines
 - * Hardware Control Language

Compsci 104 18

Finite State Machine

- $S = \{s_0, s_1, \dots, s_{n-1}\}$ is a finite set of states.
- $I = \{i_0, i_1, \dots, i_{k-1}\}$ is a finite set of input values.
- $O = \{o_0, o_1, \dots, o_{m-1}\}$ is a finite set output values.


Definition: A finite state machine is a function $F: (S \times I) \rightarrow (S \times O)$ that gets a sequence of input values $i_k \in I$, $k = 0, 1, 2, \dots$ and it produces a sequence of output values $O_k \in O$, $k = 1, 2, \dots$ such that:

$$F(s_k, i_k) = (s_{k+1}, o_{k+1}) \quad k=0, 1, 2, \dots$$

Finite State Machine (Translation to English)

- **Finite State Machine is:**
 - * A machine with a finite number of possible **states**.
 - * A machine with a finite number of possible **Inputs**.
 - * A machine with a finite number of possible different **outputs**.
 - * At each period (**Clock cycle**) the machine receives an **input** and it produces an **output**.
 - * The **output** is a function of the machine **input** and **current state**.
 - * After each period the machine changes **state**.
 - * The **new state** is a function of the **input** and **current state**.

Example: Traffic Light Controller

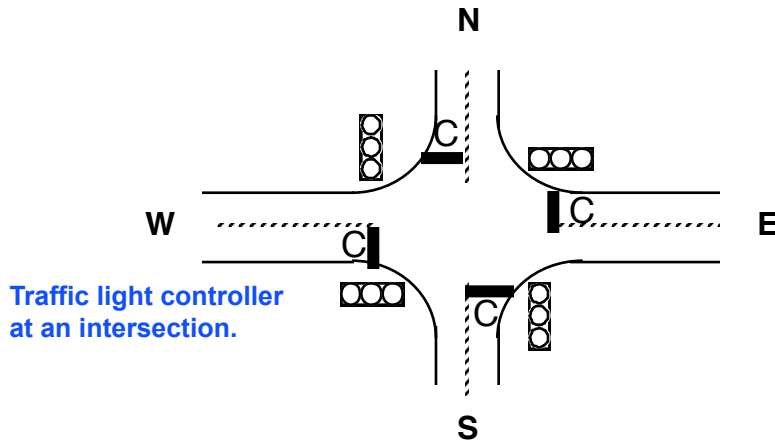

Compsci 104 21

Finite State Machine (cont.)

○ Example: Traffic lights controller:

- * There are four states:
 - NG: Green light in the north-south direction.
 - NY: Yellow light in the north-south direction.
 - EG: Green light at the East-West direction.
 - EY: Yellow light at the East-West direction.
- * There are four outputs:
 - (G;R): North-South **green light**, East-West **red light**
 - (Y;R): North-South **yellow light**, East West **red light**
 - (R;Y): North-South **red light**, East-West **yellow light**
 - (R;G): North-South **red light**, East-West **green light**
- * There are four inputs:
 - (c, c): Car at the North-South, Car at East-West
 - (c, nc) Car at North-South, No-car at East-West
 - (nc, c): No-car at North-South, Car at East-West
 - (nc, nc): No-car at North-South, No-car at East-West

Compsci 104 22

FSM Example: Traffic Light

● State Transitions:

State	Input	Next-State	Output
NG	(- ; NC)	NG	(G ; R)
NG	(- ; C)	NY	(G ; R)
NY	-	EG	(Y ; R)
EG	(NC ; -)	EG	(R ; G)
EG	(C ; -)	EY	(R ; G)
EY	-	NG	(R ; Y)

- means don't care

Format
(North/South; East/West)


Compsci 104 23

Finite State Machine (cont.)

- Finite State Machines can be represented by a graph.
- The graph is called a **State Diagram**.
- The states are the nodes in the graph.
- The arcs in the graph represent **state transitions**.
- Each arc is labeled with the **Inputs** that cause the transition
- Nodes are labeled with the **outputs**.

Compsci 104 24

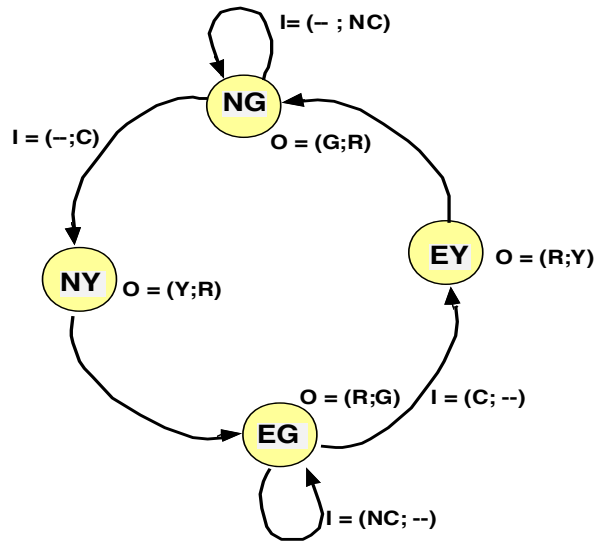FSM State Diagram Example: Traffic Light Controller



Compsci 104 25

State Coding

State	Code
NG	00
NY	01
EG	10
EY	11

Input	Code
(C; C)	11
(C; NC)	10
(NC; C)	01
(NC; NC)	00

One bit for each
Input
Input is either
true or false


Enumerate States

Output	Code
(R; G)	001100
(G; R)	100001
(Y; R)	010001
(R; Y)	001010

One bit per color for each
light
GYRGYR
(North; East)

Compsci 104 26

Coded State Diagram

 

Compsci 104 27

Example: Traffic Light Controller

S = State, bits are S0 and S1


NS = Next State, bits are NS0 and NS1

IN	S	NS	OUT
01	01	01	012345
0-	00	00	100001
1-	00	01	100001
--	01	10	010001
-0	10	10	001100
-1	10	11	001100
--	11	00	001010

$$\begin{aligned}
 NS1 &= S0' * S1' * I0 + S0 * S1' * I1 \\
 &= S1' * (S0' * I0 + S0 * I1) \\
 NS0 &= S0' * S1 + S0 * S1' * I1' + S0 * S1' * I1 \\
 &= S0' * S1 + S0 * S1' \\
 OUT0 &= S0' * S1' \\
 OUT1 &= S0' * S1 \\
 OUT2 &= S0 * S1' + S0 * S1 = S0 \\
 OUT3 &= S0 * S1' \\
 OUT4 &= S0 * S1 \\
 OUT5 &= S0' * S1' + S0' * S1 = S0'
 \end{aligned}$$

Compsci 104 28

Traffic Controller FSM implementation

 

Compsci 104 29

General Method for FSM design

- **Determine the problem:**
 1. **Draw the state diagram,**
 2. **Write the truth table,**
 3. **Write sum-of-products equations**

Compsci 104 30

A Simple Arrow FSM

- Consider those flashing arrow signs
- No light, one light, two lights, three lights
* > >> >>>
- Let's design the FSM to control this sign


Compsci 104 31

Pattern Recognizer

- A pattern recognizer examines a sequence of inputs to detect when it sees the pattern 101. When it sees this pattern its output is 1 forever.
- Let's design the FSM

Compsci 104 32

Bit Equality

 


HCL Expression

```
bool eq = (a&&b) || (!a&&!b)
```

- * Generate 1 if a and b are equal
- Hardware Control Language (HCL)
 - * Very simple hardware description language
 - Boolean operations have syntax similar to C logical operations
 - * We'll use it to describe control logic for processors

Compsci 104 33


Word Equality

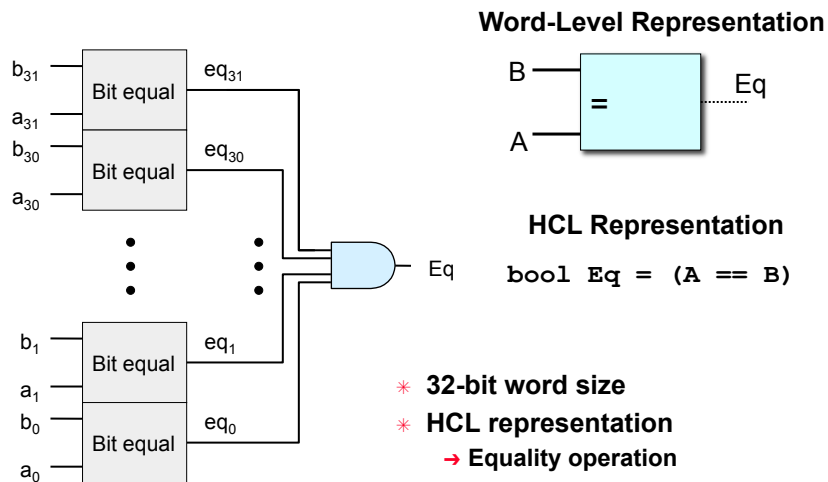

- * 32-bit word size
- * HCL representation
 - Equality operation
 - Generates Boolean value

Compsci 104 34

Bit-Level Multiplexor

 


HCL Expression

```
bool out = (s&&a) || (!s&&b)
```


- * Control signal **s**
- * Data signals **a** and **b**
- * Output **a** when **s=1**, **b** when **s=0**

Compsci 104 35

Word Multiplexor

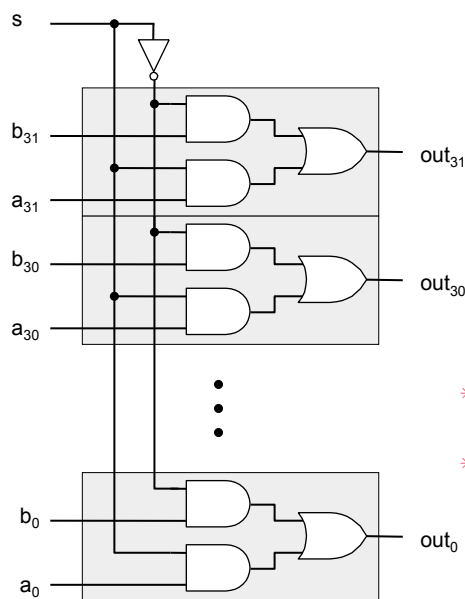

Word-Level Representation

 

HCL Representation


```
int Out = [
  s : A;
  1 : B;
];
```

- * Select input word **A** or **B** depending on control signal **s**
- * HCL representation
 - Case expression
 - Series of test : value pairs
 - Output value for first successful test

Compsci 104 36

HCL Word-Level Examples


Minimum of 3 Words

 

```
int Min3 = [
    A < B && A < C : A;
    B < A && B < C : B;
    1                : C;
];
```

- * Find minimum of three input words
- * HCL case expression
- * Final case guarantees match

4-Way Multiplexor

 


```
int Out4 = [
    !s1 && !s0 : D0;
    !s1        : D1;
    !s0        : D2;
    1          : D3;
];
```

- Select one of 4 inputs based on two control bits
- HCL case expression
- Simplify tests by assuming sequential matching

Compsci 104 37


Random-Access Memory

 

- * **Stores multiple words of memory**
 - Address input specifies which word to read or write
- * **Register file**
 - Holds values of program registers
 - %eax, %esp, etc.
 - Register identifier serves as address
 - ID 8 implies no read or write performed
- * **Multiple Ports**
 - Can read and/or write multiple words in one cycle
 - Each has separate address and data input/output

Compsci 104 38

Register File Timing

 


○ Reading

- * Like combinational logic
- * Output data generated based on input address
 - After some delay

○ Writing

 - * Like register
- * Update only as clock rises



Compsci 104 39

Summary

Finite State Machines

- Inputs, Current State
- Compute Outputs and Next State

HCL

- Language to express boolean logic
- Also, word level functions

- Homework #4

Compsci 104 40