

Basics of Logic Design: Boolean Algebra, Logic Gates

CPS 104
Lecture 8

Today's Lecture

Outline


- Building the building blocks...
- Logic Design
 - Truth tables, Boolean functions, Gates and Circuits

Reading


Appendix B, Chapter 4

The Big Picture

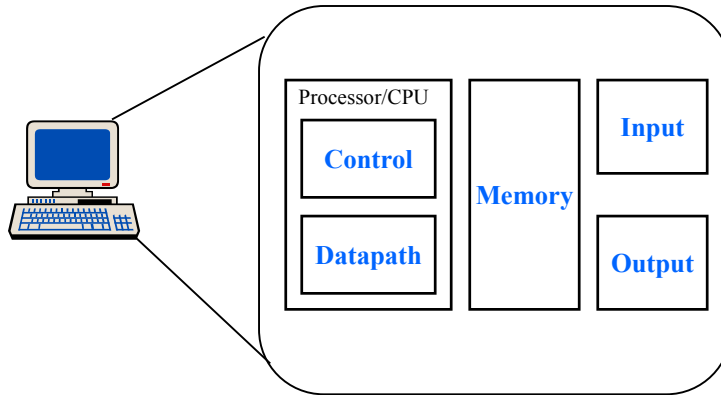- The Five Classic Components of a Computer



What We've Done, Where We're Going

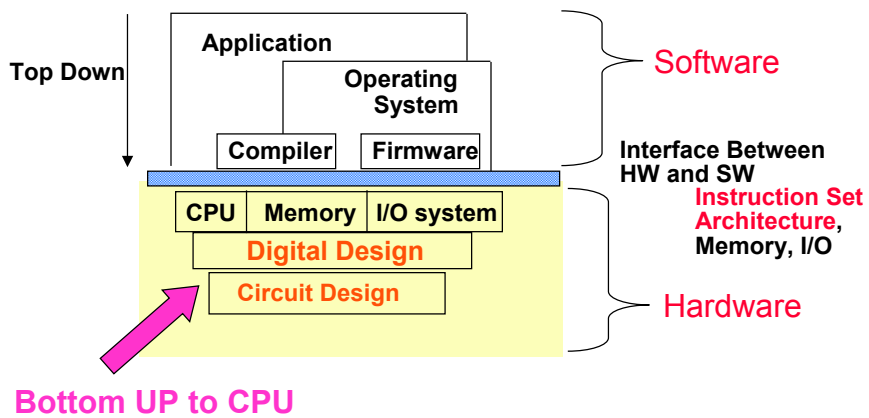

Digital Design

- Logic Design, Switching Circuits, Digital Logic

Recall: Everything is built from transistors

- A transistor is a switch
- It is either on or off
- **On** or **off** can represent **True** or **False**

Given a bunch of bits (0 or 1)...

- Is this instruction a **lw** or a **beq**?
- What register do I read?
- How do I add two numbers?
- **Need a method to reason about complex expressions**

Boolean Algebra

- Boolean functions have arguments that take two values (**{T,F}** or **{1,0}**) and they return a single or a set of (**{T,F}** or **{1,0}**) value(s).
- Boolean functions can always be represented by a table called a **“Truth Table”**
- Example: $F: \{0,1\}^3 \rightarrow \{0,1\}^2$

a	b	c	f_1, f_2
0	0	0	0 1
0	0	1	1 1
0	1	0	1 0
0	1	1	0 0
1	0	0	1 0
1	1	0	0 1
1	1	1	1 1

Boolean Functions

- **Example Boolean Functions: NOT, AND, OR, XOR, . . .**

a	NOT (a)
0	1
1	0

a	b	AND (a,b)
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR (a,b)
0	0	0
0	1	1
1	0	1
1	1	1

a	b	XOR (a,b)
0	0	0
0	1	1
1	0	1
1	1	0

a	b	XNOR (a,b)
0	0	1
0	1	0
1	0	0
1	1	1

a	b	NOR (a,b)
0	0	1
0	1	0
1	0	0
1	1	0

Boolean Functions and Expressions

- **Boolean algebra notation:** Use * for AND, + for OR, ~ for NOT.

➤ Not is also written as A' and \bar{A}

- Using the above notation we can write Boolean expressions for functions

$$F(A, B, C) = (A * B) + (\sim A * C)$$

- We can evaluate the Boolean expression with all possible argument values to construct a truth table.
- What is truth table for F?

Boolean Function Simplification

- Boolean expressions can be simplified by using the following rules:

➤ $A \cdot A = A$

➤ $A \cdot 0 = 0$

➤ $A \cdot 1 = A$

➤ $A \cdot \sim A = 0$

➤ $A + A = A$

➤ $A + 0 = A$

➤ $A + 1 = 1$

➤ $A + \sim A = 1$

➤ $A \cdot B = B \cdot A$

➤ $A \cdot (B + C) = (B + C) \cdot A = A \cdot B + A \cdot C$

Boolean Function Simplification

a	b	c	f ₁	f ₂
0	0	0	0	1
0	0	1	1	1
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	0
1	1	0	0	1
1	1	1	1	1

$$f_1 = \sim a \cdot \sim b \cdot c + \sim a \cdot b \cdot c + a \cdot \sim b \cdot c + a \cdot b \cdot c$$

$$f_2 = \sim a \cdot \sim b \cdot \sim c + \sim a \cdot \sim b \cdot c + a \cdot b \cdot \sim c + a \cdot b \cdot c$$

Simplify these functions...

Boolean Functions and Expressions

- **The Fundamental Theorem of Boolean Algebra:**
Every Boolean function can be written in disjunctive normal form as an OR of ANDs (**Sum-of products**) of its arguments or their complements.

“Proof:” Write the truth table, construct sum-of-product from the table.

a	b	XNOR (a, b)
0	0	1
0	1	0
1	0	0
1	1	1

$$\text{XNOR} = (\sim a * \sim b) + (a * b)$$

Boolean Functions and Expressions

- **Example-2:**

a	b	c	f ₁	f ₂
0	0	0	0	1
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	1	0	0	1
1	1	1	1	1

$$f_1 = \sim a * \sim b * c + \sim a * b * \sim c + a * \sim b * \sim c + a * b * c$$

$$f_2 = \sim a * \sim b * \sim c + \sim a * \sim b * c + a * b * \sim c + a * b * c$$

DeMorgan's Laws

- $\sim(A+B) = \sim A * \sim B$
- $\sim(A*B) = \sim A + \sim B$

Example:

- $\sim C * \sim A * B + \sim C * A * \sim B + C * A * B + C * \sim A * \sim B$
- Use only XOR to represent this function








Applying the Theory

- Lots of good theory
- Can reason about complex boolean expressions
- Now we have to make it real...

Boolean Gates

- **Gates** are electronic devices that implement simple Boolean functions

Examples

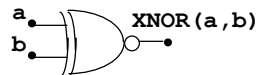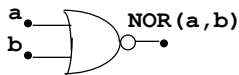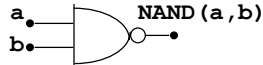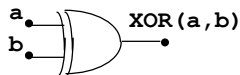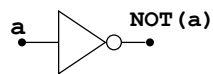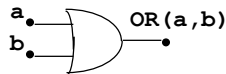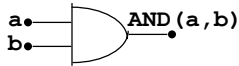

Reality Check

- **Basic 1 or 2 Input Boolean Gate 1- 4 Transistors**

Pentium III


- **Processor Core 9.5 Million Transistors**
- **Total: 28 Million Transistors**

Pentium 4


- **Total: 42 Million Transistors**

Boolean Functions, Gates and Circuits

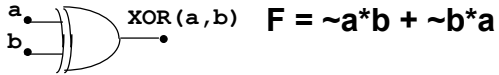- **Circuits** are made from a network of gates. (function compositions).



a	b	XOR(a, b)
0	0	0
0	1	1
1	0	1
1	1	0

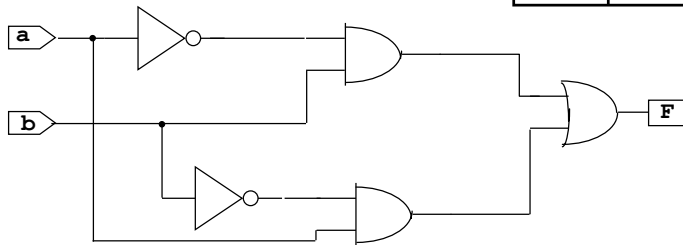

Digital Design Examples


Input: 2 bits representing an unsigned number (n)
Output: n² as 4-bit unsigned binary number

Input: 2 bits representing an unsigned number (n)
Output: 3-n as unsigned binary number

Design Example

- Consider machine with 4 registers
- Given 2-bit input (register specifier, I_1, I_0)
- Want one of 4 output bits (O_3-O_0) to be 1
 - E.g., allows a single register to be accessed
- What is the circuit for this?


Circuit Example: Decoder

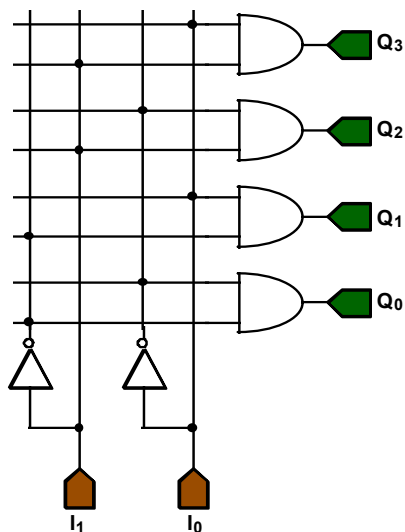


I_1	I_0	Q_0	Q_1	Q_2	Q_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Circuit Example: 2x1 MUX


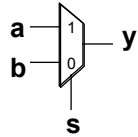
Multiplexor (MUX) selects from one of many inputs


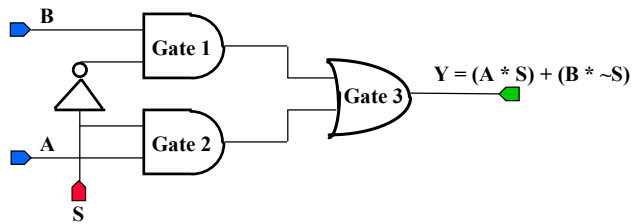
$$\text{MUX}(A, B, S) = (A * S) + (B * \sim S)$$



Example 4x1 MUX

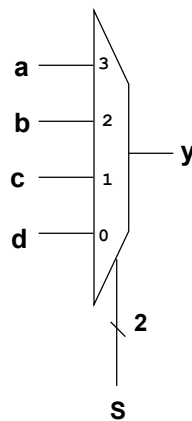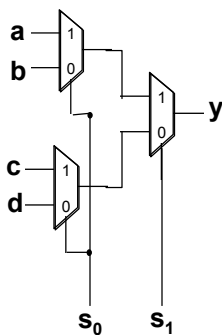

Arithmetic and Logical Operations in ISA

- What operations are there?
- How do we implement them?
 - Consider a 1-bit Adder


Summary

- Boolean Algebra & functions
- Logic gates (AND, OR, NOT, etc)
- Multiplexors

Reading

- Appendix B, Chapter 4

Example: 4-bit adder

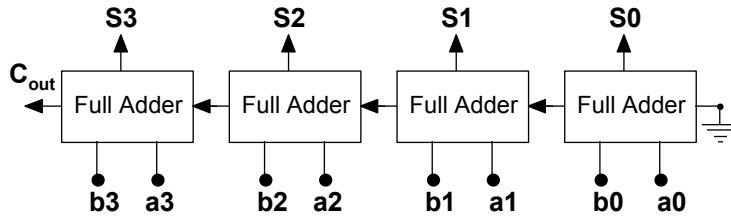

Subtraction

- How do we perform integer subtraction?
- What is the HW?

Overflow

Example1:

$$\begin{array}{r}
 0100000 \\
 \uparrow \uparrow \uparrow \uparrow \uparrow \uparrow \uparrow \\
 0110101_2 \quad (= 53_{10}) \\
 +0101010_2 \quad (= 42_{10}) \\
 \hline
 1011111_2 \quad (= -33_{10})
 \end{array}$$

Example2:

$$\begin{array}{r}
 1000000 \\
 \uparrow \uparrow \uparrow \uparrow \uparrow \uparrow \uparrow \\
 1010101_2 \quad (= -43_{10}) \\
 +1001010_2 \quad (= -54_{10}) \\
 \hline
 0011111_2 \quad (= 31_{10})
 \end{array}$$


Example3:

$$\begin{array}{r}
 1100000 \\
 \uparrow \uparrow \uparrow \uparrow \uparrow \uparrow \uparrow \\
 0110101_2 \quad (= 53_{10}) \\
 +1101010_2 \quad (= -22_{10}) \\
 \hline
 0011111_2 \quad (= 31_{10})
 \end{array}$$


Example4:

$$\begin{array}{r}
 0000000 \\
 \uparrow \uparrow \uparrow \uparrow \uparrow \uparrow \uparrow \\
 0010101_2 \quad (= 21_{10}) \\
 +0101010_2 \quad (= 42_{10}) \\
 \hline
 0111111_2 \quad (= 63_{10})
 \end{array}$$

ALU Slice

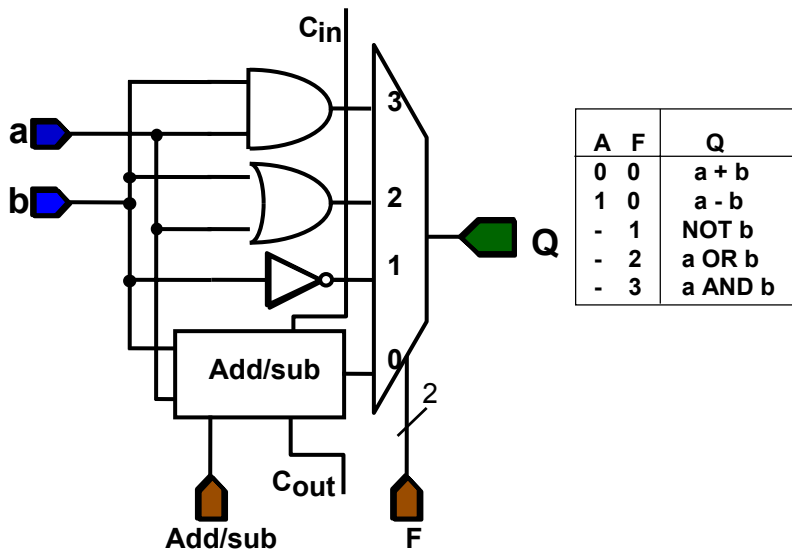

The ALU

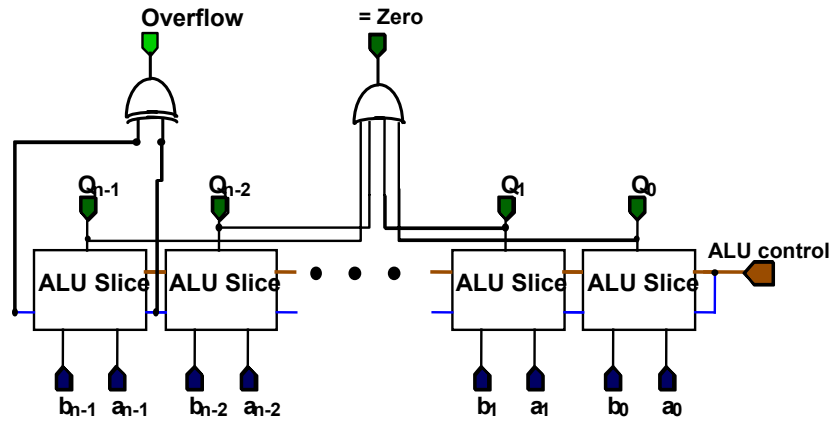

Summary

- Boolean Algebra & functions
- Logic gates (AND, OR, NOT, etc)
- Multiplexors
- Adder
- Arithmetic Logic Unit (ALU)
- Reading
- Appendix B, Chapter 4