

Basics of Logic Design Arithmetic Logic Unit (ALU)

**CPS 104
Lecture 9**

Today's Lecture

- Homework #3 Assigned Due March 3
- Project Groups assigned & posted to blackboard.
- Project Specification is on Web Due April 19
- Building the building blocks...

Outline

- Review
- Digital building blocks
- An Arithmetic Logic Unit (ALU)

Reading

Appendix B, Chapter 3

Review: Digital Design

- Logic Design, Switching Circuits, Digital Logic

Recall: Everything is built from transistors

- A transistor is a switch
- It is either on or off
- On or off can represent True or False

Given a bunch of bits (0 or 1)...

- Is this instruction a lw or a beq?
- What register do I read?
- How do I add two numbers?
- Need a method to reason about complex expressions

Review: Boolean Functions

- Boolean functions have arguments that take two values ($\{T,F\}$ or $\{0,1\}$) and they return a single or a set of ($\{T,F\}$ or $\{0,1\}$) value(s).
- Boolean functions can always be represented by a table called a “**Truth Table**”
- Example: $F: \{0,1\}^3 \rightarrow \{0,1\}^2$

a	b	c	f_1	f_2
0	0	0	0	1
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	1	0	0	1
1	1	1	1	1

Review: Boolean Functions and Expressions





$$F(A, B, C) = (A * B) + (\sim A * C)$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Review: Boolean Gates


- **Gates** are electronics devices that implement simple Boolean functions

Examples

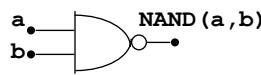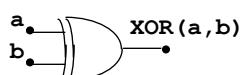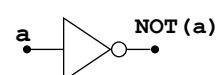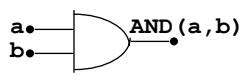


Boolean Functions, Gates and Circuits

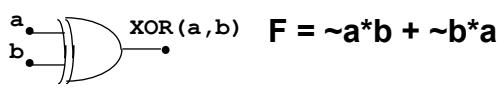- Circuits are made from a network of gates. (function compositions).



a	b	XOR(a,b)
0	0	0
0	1	1
1	0	1
1	1	0

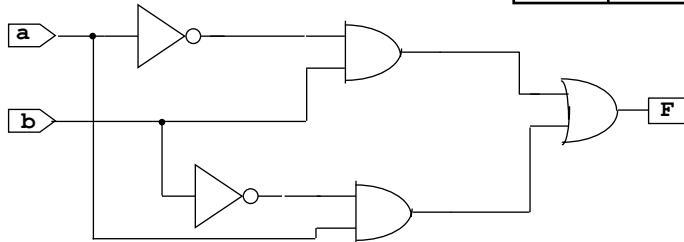

Digital Design Examples

Input: 2 bits representing an unsigned number (n)

Output: n² as unsigned binary number

Input: 2 bits representing an unsigned number (n)

Output: 3-n as unsigned binary number

More Design Examples

- **X is a 3-bit quantity**
1. Write a logic function that is true if and only if X contains at least two 1s.
 2. Implement the logic function from problem 1. using only AND, OR and NOT gates. (Note there are no constraints on the number of gate inputs.) By implement, I mean draw the circuit diagram.
 3. Write a logic function that is true if and only if X, when interpreted as an unsigned binary number, is greater than the number 5.
 4. Implement the logic function from problem 3. using only AND, OR and NOT gates. (Note there are no constraints on the number of gate inputs.)


Parity Example

- The parity code of a binary word counts the number of ones in a word. If there are an even number of ones the parity code is 0, if there are an odd number of ones the parity code is 1. For example, the parity of 0101 is 0, and the parity of 1101 is 1.
- Construct the truth table for a function that computes the parity of a **four-bit word**. Implement this function using AND, OR and NOT gates. (Note there are no constraints on the number of gate inputs.)

Design Example


- Consider machine with 4 registers
- Given 2-bit input (register specifier, I_1, I_0)
- Want one of 4 output bits (O_3-O_0) to be 1
 - E.g., allows a single register to be accessed
- What is the circuit for this?

Circuit Example: Decoder

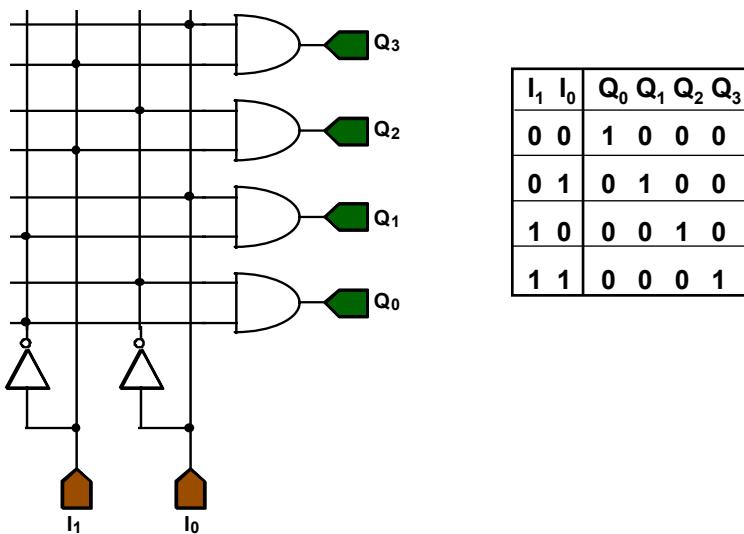


Circuit Example: 2x1 MUX


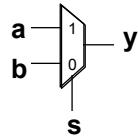
Multiplexor (MUX) **selects** from one of many inputs


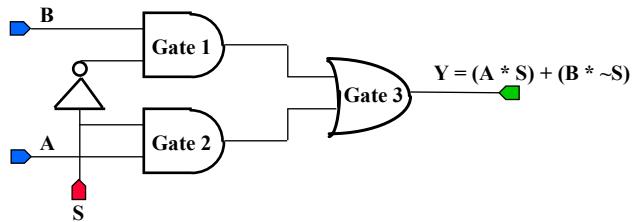
$$\text{MUX}(A, B, S) = (A * S) + (B * \sim S)$$



Example 4x1 MUX

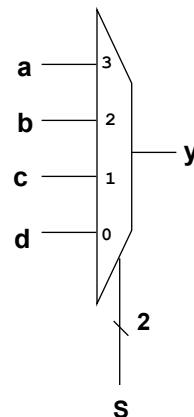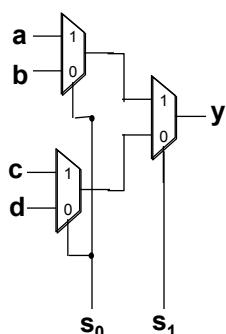

Arithmetic and Logical Operations in ISA

- What operations are there?
- How do we implement them?
 - Consider a 1-bit Adder


Truth Table for 1-bit Addition

$$\begin{array}{r} 01101100 \\ 01101101 \\ +00101100 \\ \hline 10011001 \end{array}$$

a	b	C_{in}	Sum	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

What is the circuit for Sum and for Cout?


A 1-bit Full Adder

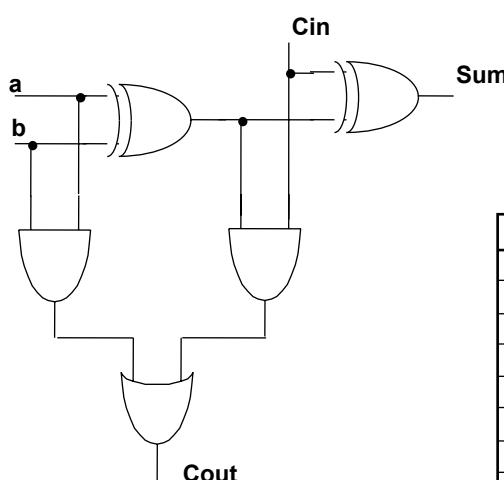


$$\begin{array}{r}
 01101100 \\
 01101101 \\
 +00101100 \\
 \hline
 10011001
 \end{array}$$

a	b	C_{in}	Sum	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Example: 4-bit adder

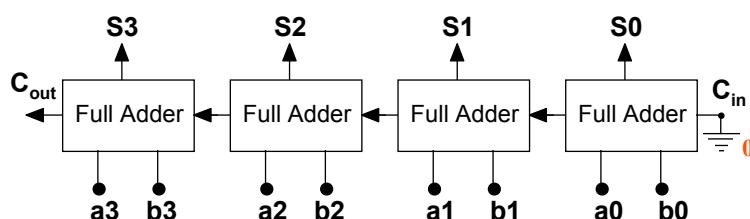

ALU Slice (Almost)

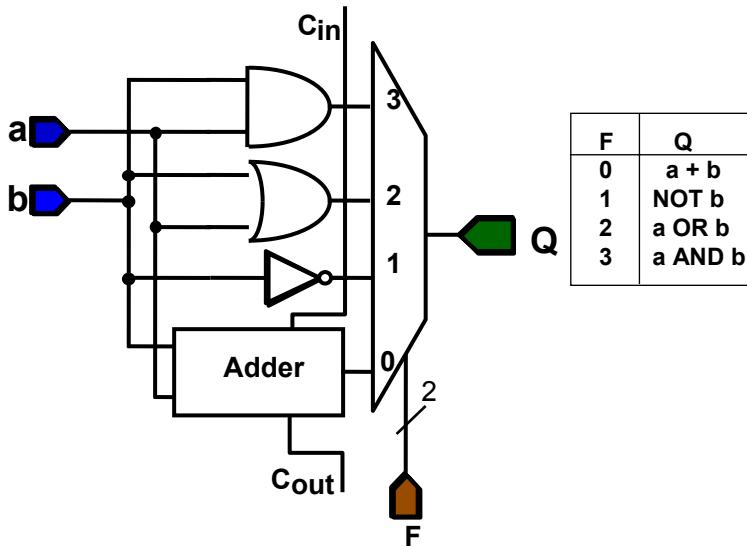

© Alvin R. Lebeck

CPS 104

19

Subtraction


- How do we perform integer subtraction?
- What is the HW?

© Alvin R. Lebeck

CPS 104

20

ALU Slice

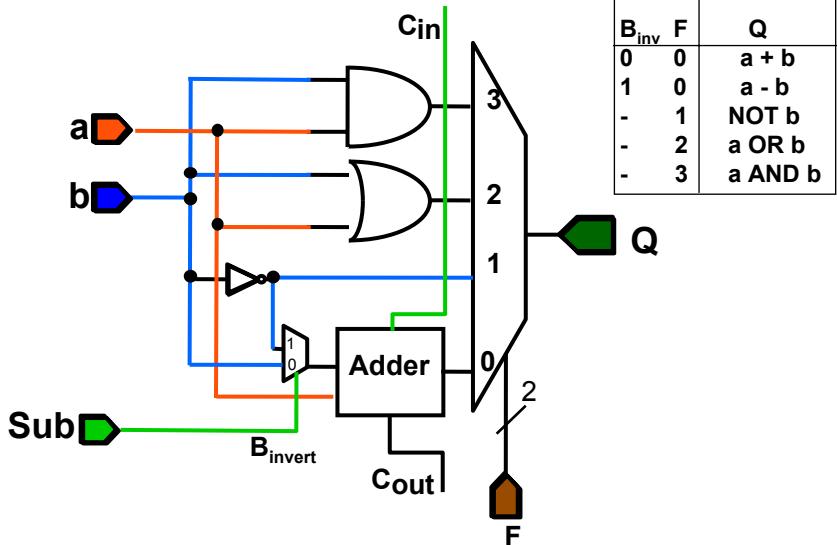


© Alvin R. Lebeck

CPS 104

21

Example: Adder/Subtractor

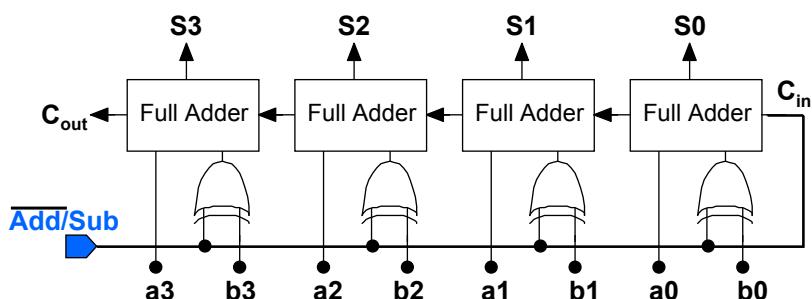

$\overline{\text{Add/Sub}} = 0 \Rightarrow \text{Addition}$
 $\overline{\text{Add/Sub}} = 1 \Rightarrow \text{Subtraction}$

© Alvin R. Lebeck

CPS 104

22

Overflow

Example1:

$$\begin{array}{r}
 01100000 \\
 0110101_2 (= 53_{10}) \\
 +0101010_2 (= 42_{10}) \\
 \hline
 1011111_2 (= -33_{10})
 \end{array}$$

Example2:

$$\begin{array}{r}
 1000000 \\
 1010101_2 (= -43_{10}) \\
 +1001010_2 (= -54_{10}) \\
 \hline
 0011111_2 (= 31_{10})
 \end{array}$$


Example3:

$$\begin{array}{r}
 11000000 \\
 0110101_2 (= 53_{10}) \\
 +1101010_2 (= -22_{10}) \\
 \hline
 0011111_2 (= 31_{10})
 \end{array}$$


Example4:

$$\begin{array}{r}
 0000000 \\
 0010101_2 (= 21_{10}) \\
 +0101010_2 (= 42_{10}) \\
 \hline
 0111111_2 (= 63_{10})
 \end{array}$$

Add/Subtract With Overflow detection

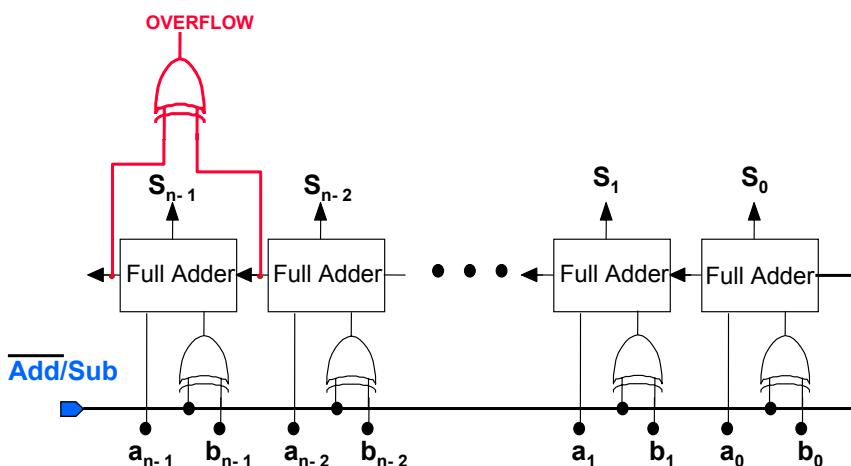

The new ALU Slice

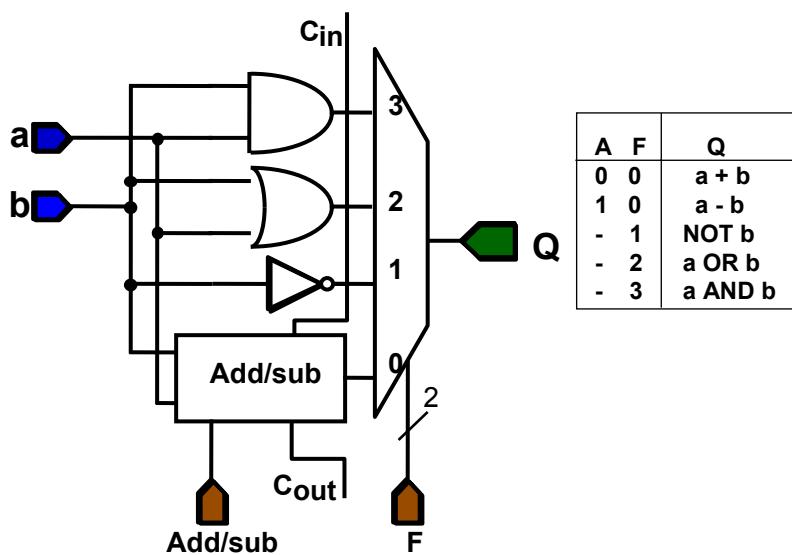


© Alvin R. Lebeck

CPS 104

25

The ALU

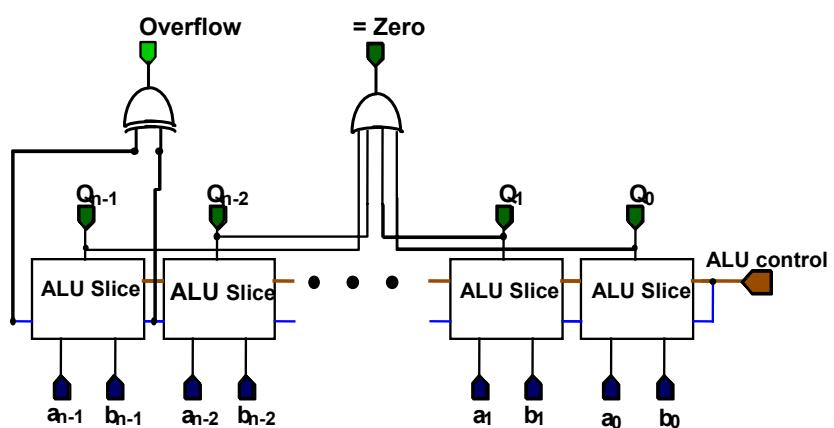


© Alvin R. Lebeck

CPS 104

26

Abstraction: The ALU

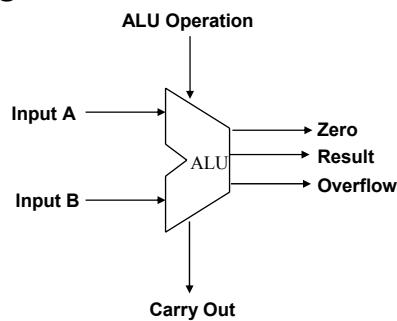
- General structure
- Two operand inputs
- Control inputs



The Shift Operation

- Consider an 8-bit machine
- How do I implement the shift operation?

Shifter

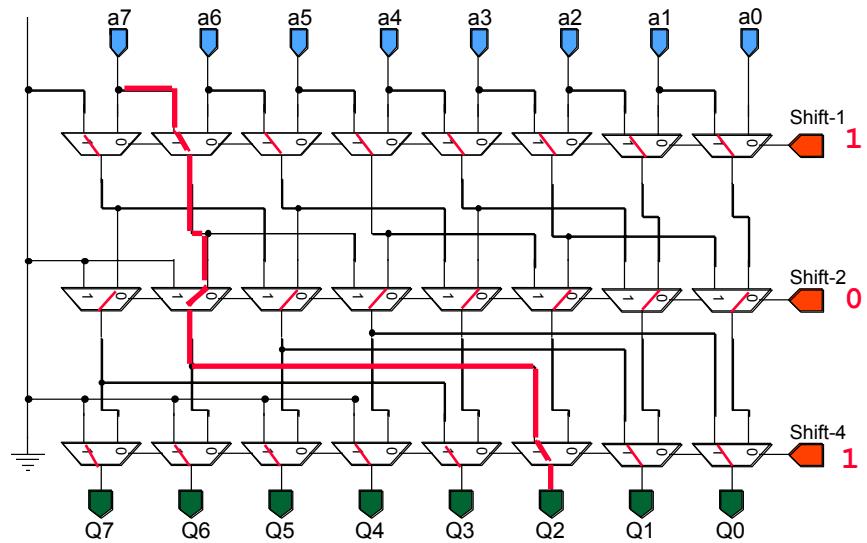

© Alvin R. Lebeck

CPS 104

29

Summary thus far

- Given Boolean function, generate a circuit that “realizes” the function.
- Constructed circuits that can **add** and **subtract**.
- The **ALU**: a circuit that can **add**, **subtract**, detect **overflow**, **compare**, and do **bit-wise operations (AND, OR, NOT)**
- Shifter

Next up: Storage Elements: Registers, Latches, Buses

© Alvin R. Lebeck

CPS 104

30